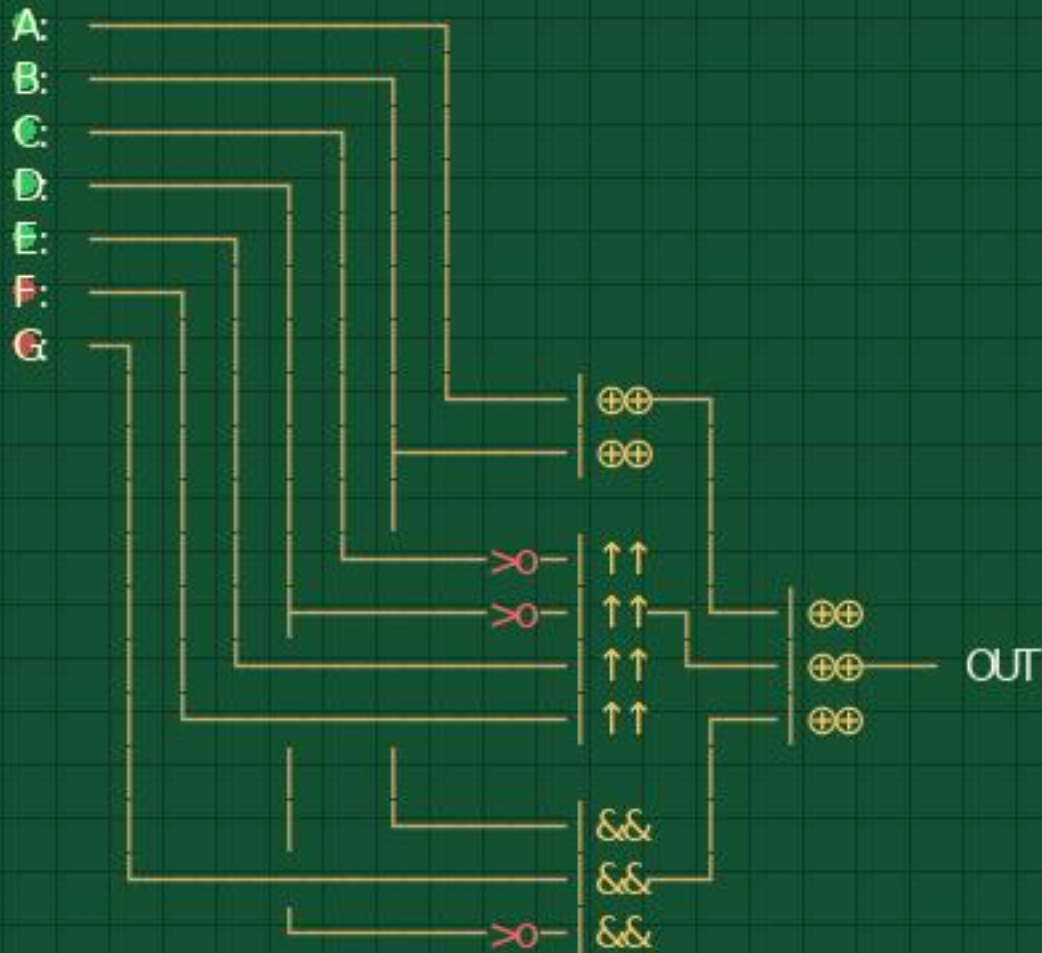


LOGIC CIRCUIT



INPUTS: ● A=1 ● B=1 ● C=1 ● D=1 ● E=1 ● F=0 ● G=0

GATES: && AND ++ OR ⊕⊕ XOR ↑↑ NAND >○ NOT

LED: ● =1(HIGH) ● =0(LOW)