

Natural Language

This problem is expressed in Natural Language.

You are given a digital logic circuit puzzle.

INPUT SIGNALS AND THEIR VALUES:

Input signal IN_0 has the value True (which is HIGH/TRUE/1) Input signal IN_1 has the value False (which is LOW/FALSE/0) Input signal IN_2 has the value True (which is HIGH/TRUE/1) Input signal IN_3 has the value False (which is LOW/FALSE/0) Input signal IN_4 has the value True (which is HIGH/TRUE/1) Input signal IN_5 has the value False (which is LOW/FALSE/0)

LOGIC GATES IN THE CIRCUIT:

The circuit contains the following logic gates, connected as described:

Gate G0 is a OR gate. This gate receives input from the following signals: IN_0, IN_5, IN_4 The output of this gate is labeled as signal G0. 2. Gate G1 is a NOT gate. This gate receives input from the following signals: IN_5 The output of this gate is labeled as signal G1. 3. Gate G2 is a NOT gate. This gate receives input from the following signals: G0 The output of this gate is labeled as signal G2. 4. Gate G3 is a OR gate. This gate receives input from the following signals: IN_5, G0 The output of this gate is labeled as signal G3. 5. Gate G4 is a NAND gate. This gate receives input from the following signals: G0, IN_2. The output of this gate is labeled as signal G4. 6. Gate G5 is a XOR gate. This gate receives input from the following signals: IN_5, IN_1. The output of this gate is labeled as signal G5.\n\n7. Gate G6 is a XOR gate. This gate receives input from the following signals: IN_5, IN_2. The output of this gate is labeled as signal G6.\n\n8. Gate G7 is a NOT gate. This gate receives input from the following signals: IN_3. The output of this gate is labeled as signal G7. 9. Gate G8 is a XOR gate. This gate receives input from the following signals: IN_4, IN_5, G3. The output of this gate is labeled as signal G8. 10. Gate G9 is a XOR gate. This gate receives input from the following signals: G2, IN_1 The output of this gate is labeled as signal G9. 11. Gate G10 is a OR gate. This gate receives input from the following signals: IN_3, G7 The output of this gate is labeled as signal G10. 12. Gate G11 is a NOR gate. This gate receives input from the following signals: G4, G5 The output of this gate is labeled as signal G11. 13. Gate G12 is a NOR gate. This gate receives input from the following signals: G10, G6, IN_4 The output of this gate is labeled as signal G12. 14. Gate G13 is a OR gate. This gate receives input from the following signals: IN_5, G11, G8. The output of this gate is labeled as signal G13. 15. Gate G14 is a NAND gate. This gate receives input from the following signals: G13, G12, IN_1. The output of this gate is labeled as signal G14. 16. Gate G15 is a NAND gate. This gate receives input from the following signals: G2, G4. The output of this gate is labeled as signal G15.

OUTPUT SIGNALS:

The final output(s) of the circuit are: G12, G14

QUESTION: If input IN_3 is flipped from False to True, how many outputs change their values?

Please carefully trace through the circuit and provide your answer as a single value (e.g., True/False for boolean outputs, or a number for counting questions)